#### CMSC 28100

# Introduction to Complexity Theory


Autumn 2025

Instructor: William Hoza



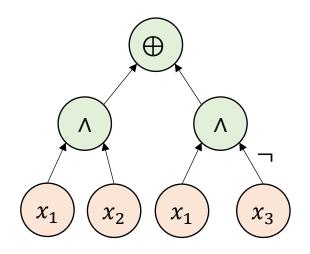
#### Boolean formulas

- Definition: An n-variate Boolean formula is a rooted binary tree
  - Each internal node is labeled with a binary logical operation
  - Each leaf is labeled with 0, 1, or a variable among  $x_1, \dots, x_n$
- It computes  $f: \{0, 1\}^n \to \{0, 1\}$
- E.g.,  $f(x_1, x_2, x_3) = (x_1 \land x_2) \oplus (x_1 \land \bar{x}_3)$


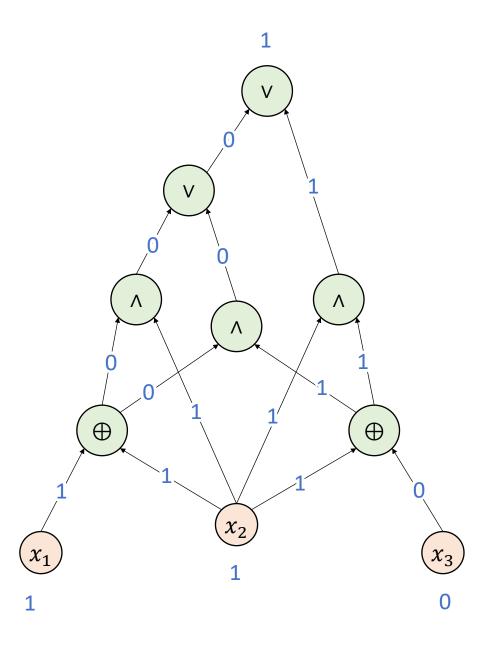
#### Boolean circuits

 A Boolean circuit is like a Boolean formula, except that we permit vertices to have multiple outgoing wires



## Boolean circuits: Rigorous definition

- **Definition:** An n-input m-output circuit is a directed acyclic graph
  - We refer to the edges as "wires"
  - Two types of nodes:
    - Each "gate" has two incoming edges and is labeled with a binary logical operation
    - ullet Otherwise, a node has zero incoming edges and is labeled with  $0,\,1,$  or a variable among  $x_1,\,...\,,x_n$
  - m of the nodes are additionally labeled as "output 1", "output 2", ..., "output m"

## Boolean circuits: Rigorous definition


- Each node g computes a function  $g: \{0, 1\}^n \to \{0, 1\}$  defined inductively:
  - If g is labeled  $x_i$ , then g(x) = the i-th bit of x
  - If g is labeled 0, then  $g(x) \equiv 0$
  - If g is labeled 1, then  $g(x) \equiv 1$
  - If g is labeled op and its incoming wires come from f and h, then g(x) = f(x) op h(x)

#### Boolean circuits

- Let the output nodes be  $g_1, \dots, g_m$
- As a whole, the circuit computes  $C: \{0,1\}^n \to \{0,1\}^m$  defined by

$$C(x) = (g_1(x), \dots, g_m(x))$$
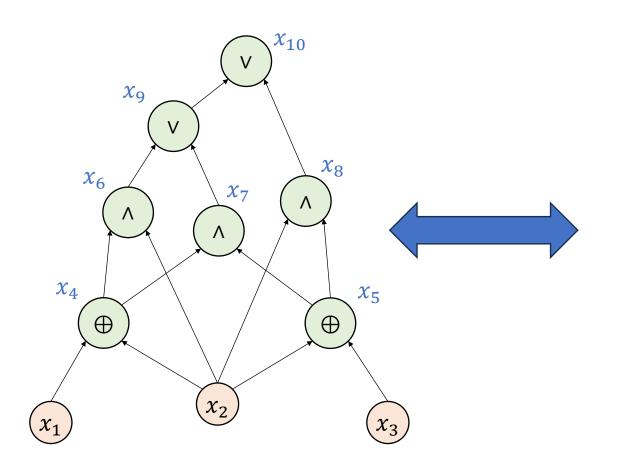
# Equivalent: Boolean straight-line programs



- $x_4 \leftarrow x_1 \oplus x_2$
- $x_5 \leftarrow x_2 \oplus x_3$
- $x_6 \leftarrow x_4 \wedge x_2$
- $x_7 \leftarrow x_4 \wedge x_5$
- $x_8 \leftarrow x_2 \land x_5$
- $x_9 \leftarrow x_6 \vee x_7$
- $x_{10} \leftarrow x_9 \vee x_8$
- Return  $x_{10}$


- Each line: Combine
   two variables, store in
   new variable
- "Return" at end
- No loops
- No "if" statements
- No branching


Circuit

Boolean Straight-Line Program

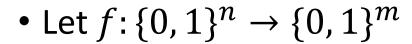
# Circuit complexity

- The size of a circuit is the total number of gates
  - How much "work" does the circuit do?



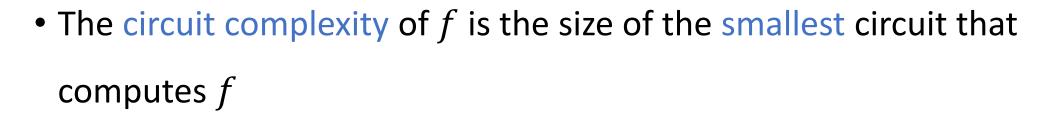


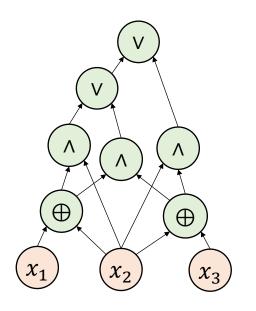• How much work is required to compute *f*?


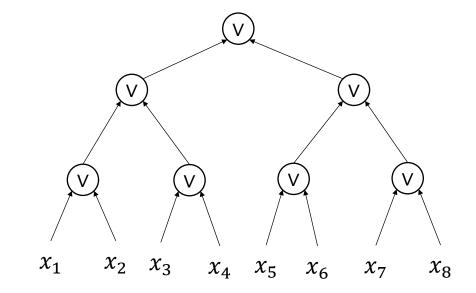
# Circuit complexity example 1

- Let  $f(x) = x_1 \lor x_2 \lor \cdots \lor x_n$
- Circuit complexity:  $\Theta(n)$





# Circuit complexity example 2

• Define  $f: \{0, 1\}^n \to \{0, 1\}$  by

 $f(x) = 1 \Leftrightarrow x$  is a palindrome

• Circuit complexity:  $\Theta(n)$ 

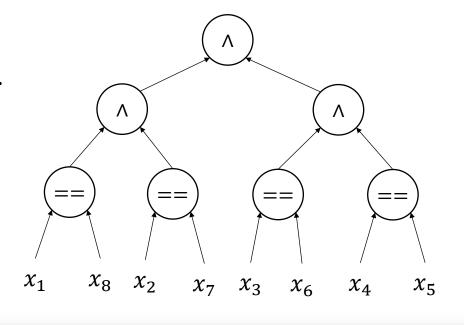

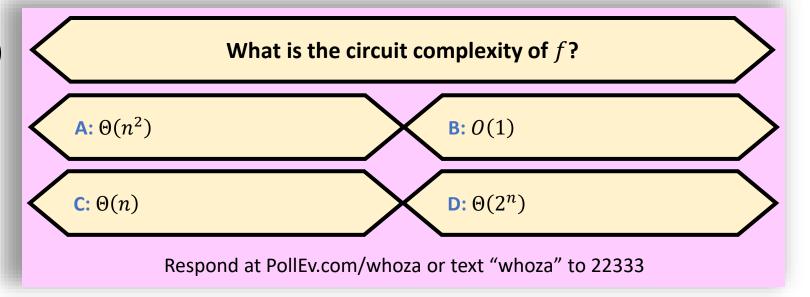

## The power of Boolean circuits

- Recall: Some languages cannot be decided by algorithms
- Are there functions that cannot be computed by circuits?

**Theorem:** For every  $f: \{0, 1\}^n \rightarrow \{0, 1\}$ , there

exists a Boolean formula that computes f.

**Theorem:** For every  $f: \{0,1\}^n \to \{0,1\}$ , there exists a Boolean formula that computes f.

- **Proof (1 slide):** For each  $z \in \{0, 1\}^n$ , construct  $T_z$  that is satisfied only by z
  - E.g.,  $T_{010} = \overline{x}_1 \wedge x_2 \wedge \overline{x}_3$

Then 
$$f(x) = \sqrt{T_z(x)}$$

$$z \in f^{-1}(1)$$

#### DNF formulas

- **Definition:** A literal is a variable or its negation  $(x_i \text{ or } \bar{x}_i)$
- **Definition:** A term is a conjunction of literals (AND of literals). Example:

$$T_{010} = \bar{x}_1 \wedge x_2 \wedge \bar{x}_3$$

• **Definition:** A disjunctive normal form (DNF) formula is a disjunction of terms (OR of ANDs of literals). Example:

$$f(x) = (\bar{x}_1 \wedge x_2 \wedge \bar{x}_3) \vee (x_1 \wedge \bar{x}_2 \wedge x_3)$$

## Every function has a DNF formula

• Let  $f: \{0, 1\}^n \rightarrow \{0, 1\}$  be any function

**Theorem:** There is a DNF formula that computes f,

with at most  $2^n$  terms and n literals per term

• **Proof:** For each  $z \in \{0,1\}^n$ , construct a term  $T_z$  that is satisfied only by z

Then 
$$f(x) = \sqrt{T_z(x)}$$
 $z \in f^{-1}(1)$ 

#### CNF formulas

• **Definition:** A clause is a disjunction of literals (OR of literals). Example:

$$C = \bar{x}_1 \vee x_2 \vee \bar{x}_3$$

• **Definition:** A conjunctive normal form (CNF) formula is a conjunction of clauses (AND of ORs of literals). Example:

$$f(x) = (\bar{x}_1 \lor x_2 \lor \bar{x}_3) \land (x_1 \lor \bar{x}_2 \lor x_3)$$

## Every function has a CNF formula

• Let  $f: \{0, 1\}^n \rightarrow \{0, 1\}$  be any function

**Theorem:** There is a CNF formula that computes f,

with at most  $2^n$  clauses and n literals per clause

- **Proof:** For each  $z \in \{0,1\}^n$ , construct a clause  $C_z$  that is violated only by z
  - E.g.,  $T_{010} = x_1 \vee \bar{x}_2 \vee x_3$

Then 
$$f(x) = \bigwedge_{z \in f^{-1}(0)} C_z(x)$$

## Multi-output functions

**Corollary:** For every  $f:\{0,1\}^n \to \{0,1\}^m$ , there exists a circuit of size  $O(m \cdot n \cdot 2^n)$  that computes f

- **Proof:** Write  $f(x) = (f_1(x), ..., f_m(x))$
- Each  $f_i$  can be computed by a circuit of size  $O(n \cdot 2^n)$  (DNF/CNF)
- Combine those m circuits into one

## Polynomial-size circuits

- Every function has a circuit
- But the circuit we constructed has exponential size 😩
- Next: Polynomial-time algorithm ⇒ polynomial-size circuits

# Circuit complexity of a binary language

- Let  $Y \subseteq \{0, 1\}^*$
- For each  $n \in \mathbb{N}$ , we define  $Y_n: \{0, 1\}^n \to \{0, 1\}$  by the rule

$$Y_n(w) = \begin{cases} 1 & \text{if } w \in Y \\ 0 & \text{if } w \notin Y \end{cases}$$

- **Definition:** The circuit complexity of Y is the function  $S: \mathbb{N} \to \mathbb{N}$  defined by  $S(n) = \text{the size of the smallest circuit that computes } Y_n$
- Note: Each circuit only handles a single input length! Different from TMs

# Turing machines vs. circuits

- Let M be a Turing machine that decides a language Y
- Let T(n) be M's time complexity; let S(n) be M's space complexity

**Theorem:** The circuit complexity of Y is  $O(T(n) \cdot S(n))$ .

Proof (next 6 slides) is based on computation histories

# Locality of computation

- Let C be a configuration of the Turing machine M
- We can write  $C = c_1 c_2 \dots c_\ell$  for some  $c_1, \dots, c_\ell \in \Sigma \cup Q$
- Then NEXT $(C) = c_1'c_2' \dots c_\ell'$  for some  $c_1', \dots, c_\ell' \in \Sigma \cup_{\circ} Q$
- Exercise 10a: If  $2 \le i \le \ell 2$ , then

$$c_i' = \begin{cases} \text{the third symbol of NEXT}(\sqcup c_{i-1}c_ic_{i+1}c_{i+2}) & \text{if } c_{i-1} \in Q \text{ or } c_i \in Q \text{ or } c_{i+1} \in Q \\ c_i & \text{otherwise} \end{cases}$$

For simplicity,

assume the


head is not at

beginning/end

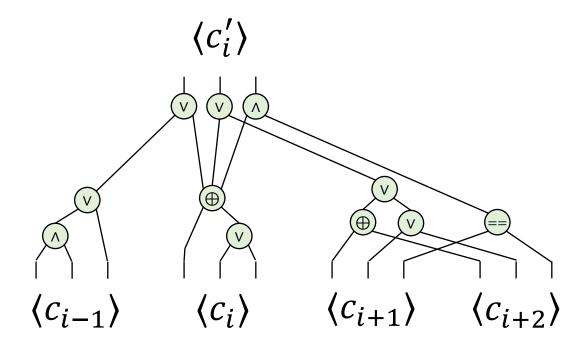
# Encoding configurations in binary

- Let C be a configuration of a TM M, say  $C=u_1u_2\dots u_kqv_1v_2\dots v_m$
- Each symbol/state  $b \in \Sigma \cup Q$  can be encoded in binary as  $\langle b \rangle \in \{0,1\}^r$  for some r = O(1)
- We define  $\langle C \rangle = \langle u_1 \rangle \langle u_2 \rangle \cdots \langle u_k \rangle \langle q \rangle \langle v_1 \rangle \cdots \langle v_m \rangle$


• There is a circuit  $C_M$  that computes  $\langle c_i' \rangle$  given  $\langle c_{i-1} \rangle$ ,  $\langle c_i \rangle$ ,  $\langle c_{i+1} \rangle$ ,  $\langle c_{i+2} \rangle$ 



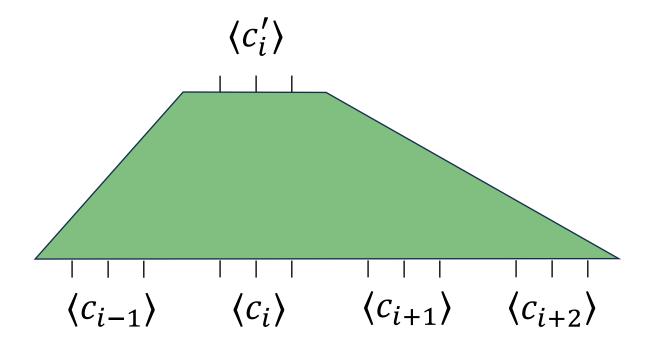
• There is a circuit  $C_M$  that computes  $\langle c_i' \rangle$  given  $\langle c_{i-1} \rangle$ ,  $\langle c_i \rangle$ ,  $\langle c_{i+1} \rangle$ ,  $\langle c_{i+2} \rangle$ 



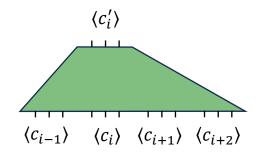• There is a circuit  $C_M$  that computes  $\langle c_i' \rangle$  given  $\langle c_{i-1} \rangle$ ,  $\langle c_i \rangle$ ,  $\langle c_{i+1} \rangle$ ,  $\langle c_{i+2} \rangle$ 



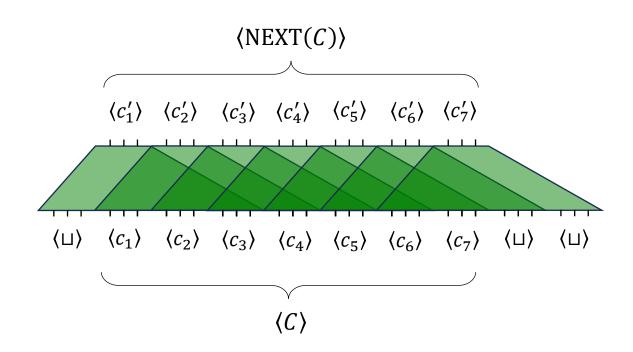• Now let's combine many copies of  $C_M$  in parallel:



- Size:  $O(S(n) \cdot T(n))$
- Assume WLOG:
  - $\langle 0 \rangle = 0^r$  and  $\langle 1 \rangle = 10^{r-1}$
  - *M* halts in starting cell
  - NEXT(C) = C if C is a halting configuration
  - $\langle q_{\rm accept} \rangle = 1^r$
  - $\langle q_{\text{reject}} \rangle = 01^{r-1}$

